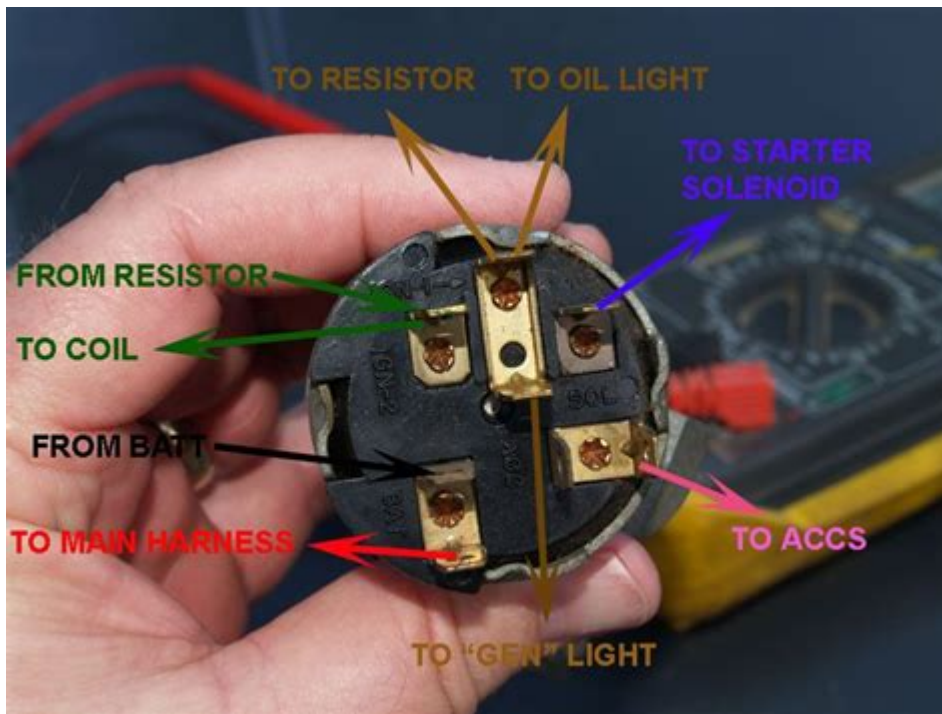


# 1955 Chevy Ignition Switch Wiring Diagram



**1955 Chevy ignition switch wiring diagram** is an essential component for any car enthusiast or mechanic working on classic Chevy models. The ignition switch is a key part of the electrical system that allows the vehicle to start and operate. Understanding the wiring diagram for the 1955 Chevy can help in diagnosing electrical issues, upgrading components, or restoring the vehicle to its original condition. This article will provide an in-depth look at the ignition switch wiring for the 1955 Chevy, including its components, wiring configurations, troubleshooting tips, and more.

## Understanding the Ignition System

The ignition system in a vehicle is responsible for igniting the fuel-air mixture in the engine's cylinders. In the 1955 Chevrolet, the ignition switch plays a crucial role in energizing this system. Here are the main components involved:

### Main Components

1. **Ignition Switch:** The device that turns the electrical circuit on or off, allowing the engine to start.
2. **Starter Solenoid:** Engages the starter motor when the ignition switch is turned to the "Start" position.
3. **Battery:** Provides the electrical power needed to start the engine and run the electrical systems.

4. Ignition Coil: Converts low voltage from the battery to high voltage required to create a spark.
5. Distributor: Distributes the high voltage from the ignition coil to the correct cylinder.

## Wiring Diagram Overview

The wiring diagram for the 1955 Chevy ignition switch typically consists of several wires connected to different components. Understanding this diagram is essential for proper installation and troubleshooting. Below is a simplified overview of the wiring diagram.

## Wiring Connections

The ignition switch in a 1955 Chevy has several terminals, each serving a specific purpose. The most common terminals are:

- Terminal 1 (Battery): Connects to the positive terminal of the battery.
- Terminal 2 (Ignition): Supplies power to the ignition coil.
- Terminal 3 (Starter): Connects to the starter solenoid.
- Terminal 4 (Accessory): Powers the electrical accessories when the key is turned to the "Acc" position.

## Typical Wiring Colors

The wiring colors can help identify the connections easily. Here is a list of common wire colors associated with the ignition switch:

- Red: Battery positive
- Brown: Ignition power
- Yellow: Starter solenoid
- Pink: Accessory power

## Wiring Steps for Installation

To install or replace the ignition switch in a 1955 Chevy, follow these steps:

## Tools Required

- Screwdrivers (flathead and Phillips)
- Wire cutters/strippers

- Pliers
- Soldering iron (optional)
- Electrical tape
- Multimeter (for testing)

## Step-by-Step Installation

1. Disconnect the Battery: Always start by disconnecting the negative terminal of the battery to prevent any electrical shock or short circuits.
2. Remove the Old Ignition Switch: Unscrew the ignition switch from the dashboard and disconnect the wiring harness.
3. Identify and Label Wires: Before disconnecting, label each wire according to its terminal to simplify reconnection.
4. Connect the New Ignition Switch:
  - Connect the red wire to Terminal 1 (Battery).
  - Connect the brown wire to Terminal 2 (Ignition).
  - Connect the yellow wire to Terminal 3 (Starter).
  - Connect the pink wire to Terminal 4 (Accessory).
5. Secure the Ignition Switch: Once all wires are connected, secure the ignition switch back into the dashboard.
6. Reconnect the Battery: Reconnect the negative terminal of the battery.
7. Test the Ignition Switch: Turn the key to check if the vehicle starts and all accessories work properly.

## Troubleshooting Common Problems

If you experience issues with the ignition switch or starting the vehicle, several common problems may arise. Here are some troubleshooting tips:

### Symptoms of a Faulty Ignition Switch

- Car does not start when the key is turned.
- Accessories do not power up.
- Flickering lights when turning the key.
- The engine starts but dies immediately.

## Troubleshooting Steps

1. Check the Battery: Ensure the battery is charged and the connections are secure.
2. Inspect Wiring Connections: Look for any loose or corroded connections, especially at the ignition switch and battery.
3. Test the Ignition Switch: Use a multimeter to check for continuity in the ignition switch. If it fails, consider replacing it.
4. Examine the Starter Solenoid: If the ignition switch is functioning but the engine does not crank, test the starter solenoid.

5. Look for Ground Issues: Ensure that the ground connections are secure and free of corrosion.

## **Upgrading the Ignition System**

Many enthusiasts choose to upgrade their ignition systems for better performance and reliability. Here are some popular upgrade options:

### **High-Performance Ignition Coil**

- Upgrading to a high-performance ignition coil can provide a more powerful spark, improving engine performance and efficiency.

### **Electronic Ignition Conversion**

- Converting from points to an electronic ignition system can reduce maintenance and improve reliability. This upgrade usually includes a new ignition module and distributor.

### **Wiring Harness Upgrade**

- A new wiring harness can reduce voltage drop and improve the overall electrical performance of the vehicle.

## **Conclusion**

The 1955 Chevy ignition switch wiring diagram is a fundamental resource for anyone working on this classic vehicle. Understanding the components, wiring connections, and troubleshooting techniques is crucial for maintaining and restoring the vehicle to its original glory. Whether you are a seasoned mechanic or a novice enthusiast, having a good grasp of the ignition system will ensure that your 1955 Chevy runs smoothly and reliably. Remember to follow proper safety procedures when working with electrical systems and consult a professional if you encounter complex issues.

## **Frequently Asked Questions**

### **What is the purpose of the ignition switch in a 1955 Chevy?**

The ignition switch in a 1955 Chevy controls the electrical power to the

ignition system, allowing the engine to start and run.

## **Where can I find a wiring diagram for the 1955 Chevy ignition switch?**

Wiring diagrams for the 1955 Chevy ignition switch can be found in service manuals, online automotive forums, and classic car restoration websites.

## **What are the main components involved in the ignition switch wiring of a 1955 Chevy?**

The main components include the ignition switch itself, the battery, the starter solenoid, and the ignition coil.

## **How can I troubleshoot ignition switch wiring issues in a 1955 Chevy?**

To troubleshoot, check for continuity in the wires, inspect the ignition switch for faults, and verify connections to the battery and ignition coil.

## **What color wires are typically used in the ignition switch wiring of a 1955 Chevy?**

Common wire colors include red for battery power, yellow for the starter, and brown for the ignition circuit, but it can vary by vehicle.

## **Is it difficult to replace the ignition switch in a 1955 Chevy?**

Replacing the ignition switch in a 1955 Chevy is relatively straightforward, but it requires basic automotive electrical knowledge and tools.

## **Can I use a modern ignition switch with my 1955 Chevy?**

Yes, you can use a modern ignition switch, but you may need to adapt the wiring and ensure compatibility with the original electrical system.

## **What tools do I need to work on the ignition switch wiring of a 1955 Chevy?**

You will need basic tools such as a multimeter, wire strippers, crimping tools, and a screwdriver set to work on the ignition switch wiring.

## **Are there any common problems with the ignition switch wiring in a 1955 Chevy?**

Common problems include corroded connections, broken wires, and faulty

ignition switches that can prevent the vehicle from starting.

Find other PDF article:

<https://soc.up.edu.ph/25-style/Book?docid=lqa73-1402&title=goodman-furnace-troubleshooting-guide.pdf>

## **1955 Chevy Ignition Switch Wiring Diagram**

### **1955 - Wikipedia**

1955 (MCMLV) was a common year starting on Saturday of the Gregorian calendar, the 1955th year of the Common Era (CE) and Anno Domini (AD) designations, the 955th year of the 2nd ...

### *What Happened in 1955 - On This Day*

What happened and who was famous in 1955? Browse important and historic events, world leaders, famous birthdays and notable deaths from the year 1955.

### 1955: what happened that year? | TakeMeBack.to

Relive the key moments of 1955! From political shifts to cultural breakthroughs, discover the most significant events that shaped the year.

### **1955 Events & Facts - Baby Boomers**

What Happened in 1955? Be the first to comment on this article.

### 26 Facts About 1955 - OhMyFacts

Jun 18, 2025 · Discover 26 fascinating facts about the year 1955, from historical events to cultural milestones that shaped the world. Dive into the past!

### *Top 10 Biggest Events of the Year 1955 - TheTopTens*

So which events defined the chaos and curiosity of 1955 for you? Which ones sent shockwaves across continents or quietly altered the course of your everyday life?

### **What Happened In 1955 - Historical Events 1955 - EventsHistory**

Dec 10, 2016 · What happened in the year 1955 in history? Famous historical events that shook and changed the world. Discover events in 1955.

### **Year 1955 Fun Facts, Trivia, and History - HubPages**

Aug 4, 2021 · This article teaches you fun facts, trivia, and history events from the year 1955. Find out about popular TV shows, movies, music, books, foods, sports facts, famous birthdays, and ...

### Historical Events in 1955 - On This Day

Historical events from year 1955. Learn about 464 famous, scandalous and important events that happened in 1955 or search by date or keyword.

### **1955 Annual History Facts - History in Popular Culture**

When Albert Einstein died in 1955, the physician who conducted his autopsy at Princeton stole his

brain and took it home to perform "research," for which he was ultimately fired after refusing to ...

### *1955 - Wikipedia*

1955 (MCMLV) was a common year starting on Saturday of the Gregorian calendar, the 1955th year of the Common Era (CE) and Anno Domini (AD) designations, the 955th year of the 2nd ...

### What Happened in 1955 - On This Day

What happened and who was famous in 1955? Browse important and historic events, world leaders, famous birthdays and notable deaths from the year 1955.

### **1955: what happened that year? | TakeMeBack.to**

Relive the key moments of 1955! From political shifts to cultural breakthroughs, discover the most significant events that shaped the year.

### **1955 Events & Facts - Baby Boomers**

What Happened in 1955? Be the first to comment on this article.

### **26 Facts About 1955 - OhMyFacts**

Jun 18, 2025 · Discover 26 fascinating facts about the year 1955, from historical events to cultural milestones that shaped the world. Dive into the past!

### Top 10 Biggest Events of the Year 1955 - TheTopTens

So which events defined the chaos and curiosity of 1955 for you? Which ones sent shockwaves across continents or quietly altered the course of your everyday life?

### **What Happened In 1955 - Historical Events 1955 - EventsHistory**

Dec 10, 2016 · What happened in the year 1955 in history? Famous historical events that shook and changed the world. Discover events in 1955.

### **Year 1955 Fun Facts, Trivia, and History - HubPages**

Aug 4, 2021 · This article teaches you fun facts, trivia, and history events from the year 1955. Find out about popular TV shows, movies, music, books, foods, sports facts, famous birthdays, and ...

### *Historical Events in 1955 - On This Day*

Historical events from year 1955. Learn about 464 famous, scandalous and important events that happened in 1955 or search by date or keyword.

### 1955 Annual History Facts - History in Popular Culture

When Albert Einstein died in 1955, the physician who conducted his autopsy at Princeton stole his brain and took it home to perform "research," for which he was ultimately fired after refusing to ...

"Unlock the secrets of your classic ride with our comprehensive 1955 Chevy ignition switch wiring diagram. Learn how to wire it correctly today!"

[Back to Home](#)