
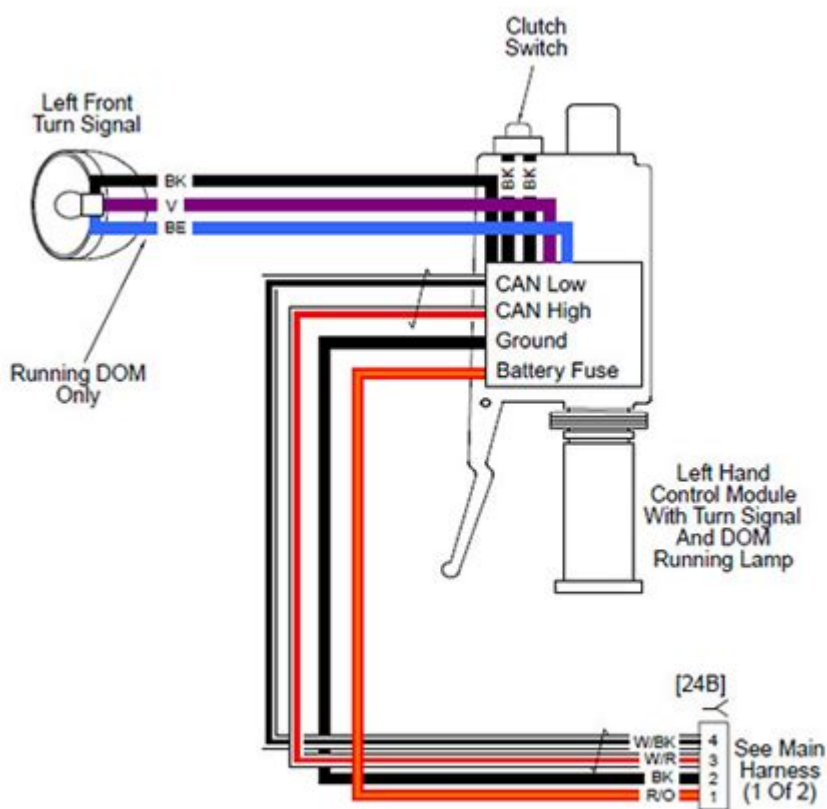


3 Wire Harley Turn Signal Wiring Diagram

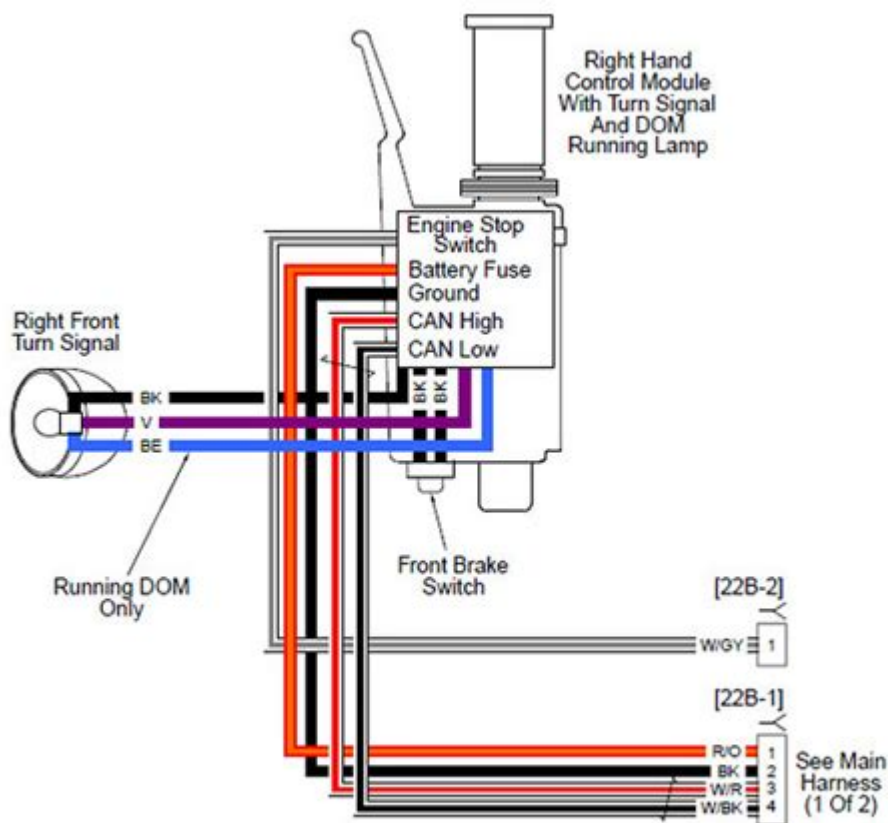

Front Lighting and Hand Controls: 2013 Softail

3 wire harley turn signal wiring diagram is an essential topic for any Harley-Davidson motorcycle owner looking to upgrade or troubleshoot their turn signal systems.

Understanding how to properly wire turn signals is crucial for ensuring safety and compliance with traffic laws. This article will provide you with a comprehensive guide to the 3-wire turn signal system, including wiring diagrams, common issues, and troubleshooting tips.

Understanding the 3 Wire Turn Signal System

The 3-wire turn signal system is a common configuration found in many Harley-Davidson motorcycles. This setup typically includes three wires for each turn signal:

- **Power (Positive)**
- **Ground (Negative)**
- **Signal (Control)**

The power wire delivers electricity to the turn signal, the ground wire completes the circuit back to the battery, and the signal wire connects to the motorcycle's turn signal switch. Understanding each wire's function is key to troubleshooting and making any necessary modifications.

Wiring Diagram for 3 Wire Harley Turn Signals

When working with a 3-wire turn signal system, having a wiring diagram is invaluable. Below is a basic representation of how these wires connect in a typical Harley setup:

Diagram Overview

- **Power Wire** (usually colored green): This wire connects directly to the battery or the fuse box. It supplies power to the turn signal bulbs.
- **Ground Wire** (typically black): This wire connects to the motorcycle's frame, providing a return path for electricity.
- **Signal Wire** (often yellow or orange): This wire connects to the turn signal switch, allowing the rider to control when the turn signals are activated.

Basic Wiring Steps

1. **Locate the Turn Signal Wiring Harness:** The first step is to find the wiring harness that

connects to your turn signals. This is usually located near the handlebars or rear fender.

2. Identify the Wires: Use a multimeter to identify which wires correspond to power, ground, and signal. Refer to your motorcycle's service manual for specific wire colors if needed.

3. Connect the Wires:

- Connect the power wire from the harness to the positive terminal of the turn signal.
- Connect the ground wire from the harness to the negative terminal of the turn signal.
- Finally, connect the signal wire to the appropriate terminal on the turn signal.

4. Secure Connections: Use electrical tape or heat shrink tubing to protect your connections from moisture and dirt.

5. Test the Signal: Once everything is connected, turn on your motorcycle and activate the turn signal switch. Check to ensure the lights are functioning correctly.

Common Issues with 3 Wire Harley Turn Signals

While the 3-wire turn signal system is generally reliable, issues can arise. Here are some common problems and their solutions:

1. Turn Signals Not Working

If your turn signals are not functioning, the issue could be related to:

- Faulty Bulbs: Check if the bulbs are burned out and replace them if necessary.
- Bad Ground Connection: Ensure that the ground wire is securely connected to the frame and free of rust or paint.
- Broken Signal Wire: Inspect the signal wire for any damage or breaks, especially near the handlebars.

2. Turn Signals Blink Too Fast or Too Slow

If your turn signals are blinking at an irregular rate, it could indicate a problem with the flasher relay or the bulbs:

- Incorrect Bulb Wattage: Ensure that you are using the correct wattage bulbs as specified in your motorcycle manual.
- Flasher Relay Issues: A malfunctioning relay can cause erratic blinking. Consider replacing it if you suspect it's the issue.

3. Turn Signals Stay On Continuously

When turn signals do not turn off, check the following:

- Faulty Switch: The turn signal switch may be stuck or malfunctioning. Inspect or replace if necessary.
- Wiring Short: Look for any signs of a short circuit in the wiring that might keep the signal active.

Upgrading to LED Turn Signals

Many Harley-Davidson owners choose to upgrade their turn signals to LED for better visibility and energy efficiency. If you decide to make this upgrade, remember that LED bulbs may require a load resistor or a new flasher relay to function correctly.

Steps for Upgrading to LED Turn Signals

1. Purchase Compatible LED Bulbs: Ensure the bulbs are compatible with your motorcycle's turn signal housing.
2. Remove Old Bulbs: Carefully remove the old incandescent bulbs from the sockets.
3. Install LED Bulbs: Insert the new LED bulbs into the sockets.
4. Add Load Resistors (if necessary): If the turn signals blink too quickly, you may need to install load resistors to simulate the load of conventional bulbs.
5. Test the Turn Signals: After installation, activate the turn signals to ensure they function properly.

Conclusion

Understanding the **3 wire harley turn signal wiring diagram** is crucial for any Harley owner looking to maintain or upgrade their motorcycle's lighting system. By following the steps outlined in this article, you can troubleshoot common issues and perform basic wiring tasks with confidence. Whether you're replacing old bulbs, upgrading to LED, or simply ensuring your turn signals work correctly, having a solid grasp of the wiring diagram and connections will keep you safe on the road. Always consult your service manual and, when in doubt, seek professional assistance to ensure your motorcycle remains in top condition.

Frequently Asked Questions

What is a 3 wire Harley turn signal wiring diagram used for?

A 3 wire Harley turn signal wiring diagram is used to connect and configure the turn signal lights on Harley-Davidson motorcycles, ensuring proper functionality for signaling during rides.

What are the three wires in a 3 wire Harley turn signal setup?

The three wires typically include a positive wire (for power), a negative wire (for ground), and a signaling wire (to activate the turn signal light).

How do you wire a 3 wire Harley turn signal?

To wire a 3 wire Harley turn signal, connect the positive wire to the turn signal switch, the ground wire to the motorcycle's frame, and the signaling wire to the corresponding left or right turn signal circuit.

What should I do if my 3 wire Harley turn signal is not working?

If your 3 wire Harley turn signal is not working, check the connections for any loose or damaged wires, ensure the bulbs are functioning, and verify that the turn signal switch is operational.

Can I use a 3 wire turn signal on a motorcycle with a different wiring system?

Using a 3 wire turn signal on a motorcycle with a different wiring system may require additional modifications or an adapter, as the wiring configuration and function may vary between models.

Find other PDF article:

<https://soc.up.edu.ph/44-slide/pdf?ID=EHR84-0824&title=number-tracing-worksheets-1-100.pdf>

[3 Wire Harley Turn Signal Wiring Diagram](#)

2025 7月 30日 星期三 RTX 5060

Jun 30, 2025 · 1080P/2K/4K RTX 5060 25日

10 ...

8 Gen3 8 ? -
8 Gen3 1+5+2 1 Prime 3.3GHz5 Performance
3.2GHz2 Efficiency ...

-
2011 1
...

-
1. January Jan2. February Feb3. March Mar4. April Apr5. May
May6. June Jun7. July Jul8. ...

10 -
GB120.1-20104500W1233.63.43.2
10 ...

Google Gemma-3 -
Gemma 3 +
...

"Discover how to simplify your bike's setup with our comprehensive 3 wire Harley turn signal wiring diagram. Get clear instructions and tips—learn more now!"

[Back to Home](#)